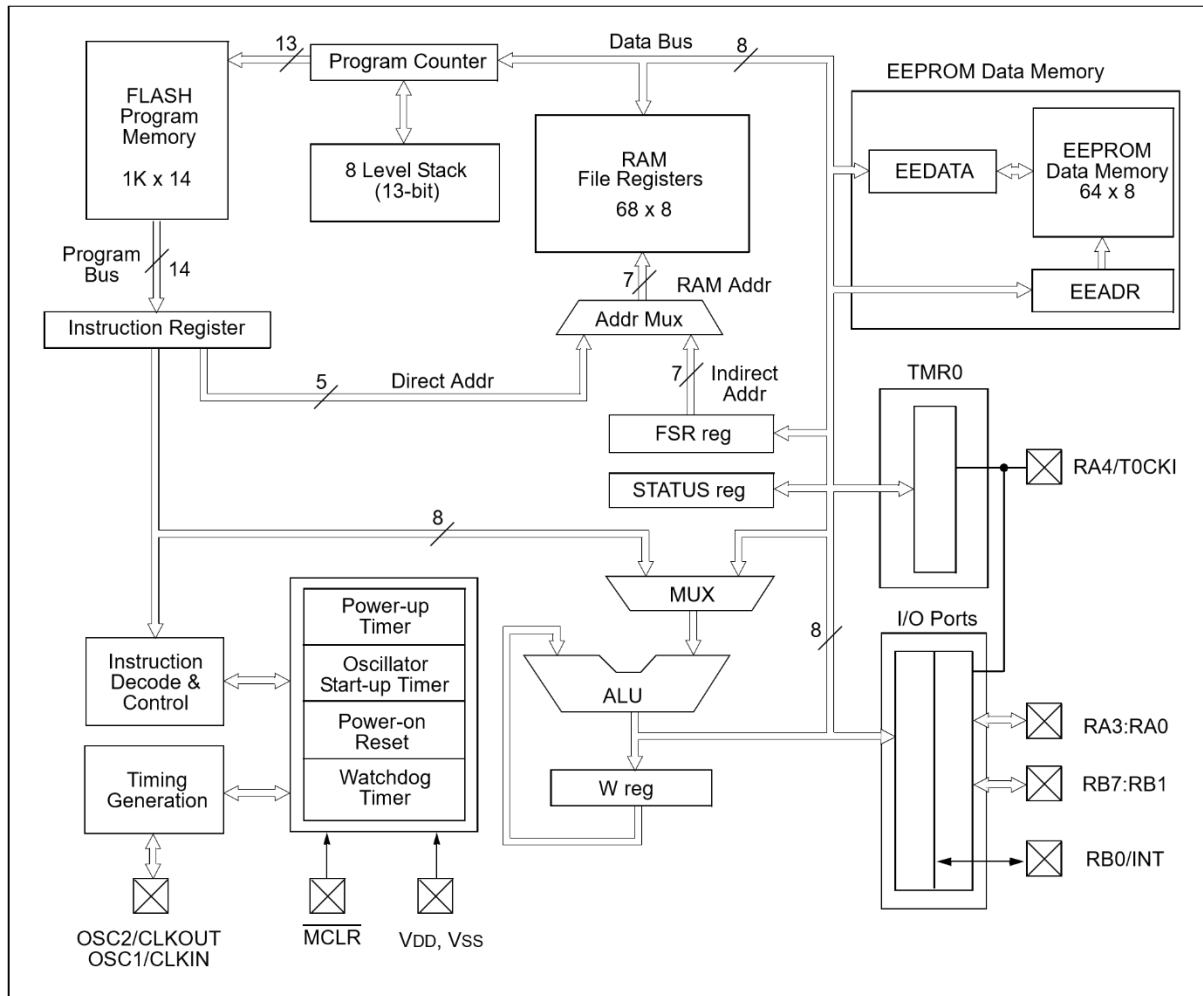


Internal Architecture of the PIC16F84A



Main Processor

Consists of three main blocks:

- Multiplexer (MUX)
- Watchdog Timer (WDT)
- Arithmetic Logic Unit (ALU)

Architecture

- RISC type (Reduced Instruction Set Computer)
 - 14-bit operation code (Opcode)
-

Memory

- Two types of registers:
 - **SFR** (Special Function Registers)
 - **GPR** (General Purpose Registers)
 - Two banks with twelve registers each, 14 bits per register
-

Interface

- **(MCLR)** – Master Clear (Reset) pin with inversion.
Used to reset the program counter (PC - Program Counter).
 - **PORTA** – 8-bit port, but only the lower 5 bits are used, resulting in 5 physical pins.
 - **PORTB** – 8-bit port that uses all 8 bits, providing 8 physical pins.
-

Stack Memory

- 8 levels, each with 13 cells → 8×13
-

Oscillator

- Quartz Crystal Resonator (XT_OSC) – 32 KHz
 - Capacitor C1: 100 nF
 - Capacitor C2: 22 pF
 - Capacitor C3: 22 pF
-

Power Supply

- Power source (VDD)
- Ground (VSS)

TMR0

TMR0 – Timer 0 is an 8-bit register whose purpose is to count from 0 to 255. This generates a precisely defined operating frequency for Timer 0 overflow. When the timer is initially reset and the operating frequency of the quartz resonator and the division coefficient of Timer 0 are determined, their values are used in the formula:

From 256, the value of TMR0, which is reset by the program, is subtracted. This result is then multiplied by **1 divided by the division coefficient (Kdel)**, which is set by the program, and further multiplied by **1 divided by the oscillator frequency (Fosc)**, which is set using a quartz resonator (XT_OSC) with a value of **32 KHz**. This determines the time period for which TMR0 overflows from 0 to 255.

Division Coefficients

OPTION_REG

```
| RP0 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 |  
| RP1 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 |  
| RP2 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 |
```

```
| Division Ratio | 1:2 | 1:4 | 1:8 | 1:16 | 1:32 | 1:64 | 1:128 | 1:256 |
```

$$TI = (256 - (TMR0)) * (1 / Kdiv) * (4 / Fosc)$$

$$(256 - 0) * (1 / 32) * (4 / 32,768)$$



$$256 * (1 / 32) * (4 / 32,768)$$

$$8 * (4 / 32,768) = 32 / 32,768 = 0.0009765625 \text{ seconds}$$

(or 976.56 microseconds)

This means the timer overflows: $1 / 0.0009765625 = 1024$ times per second (1024 Hz)


Block Diagram

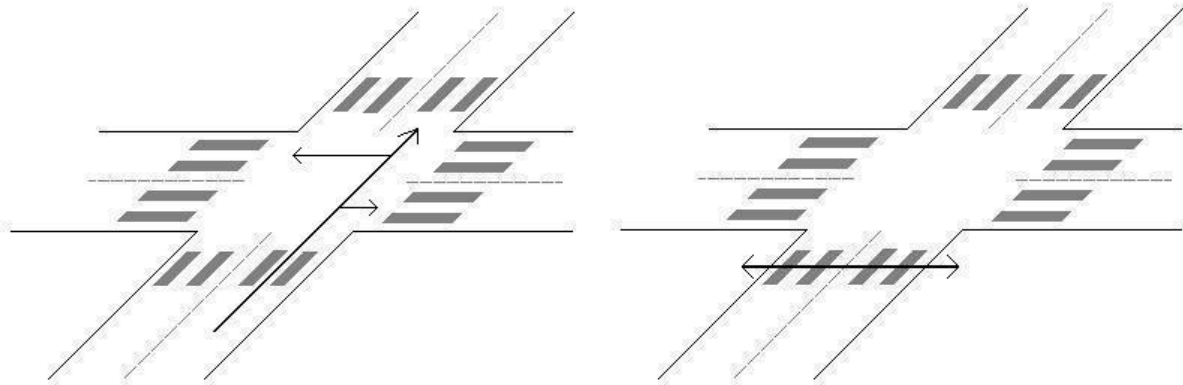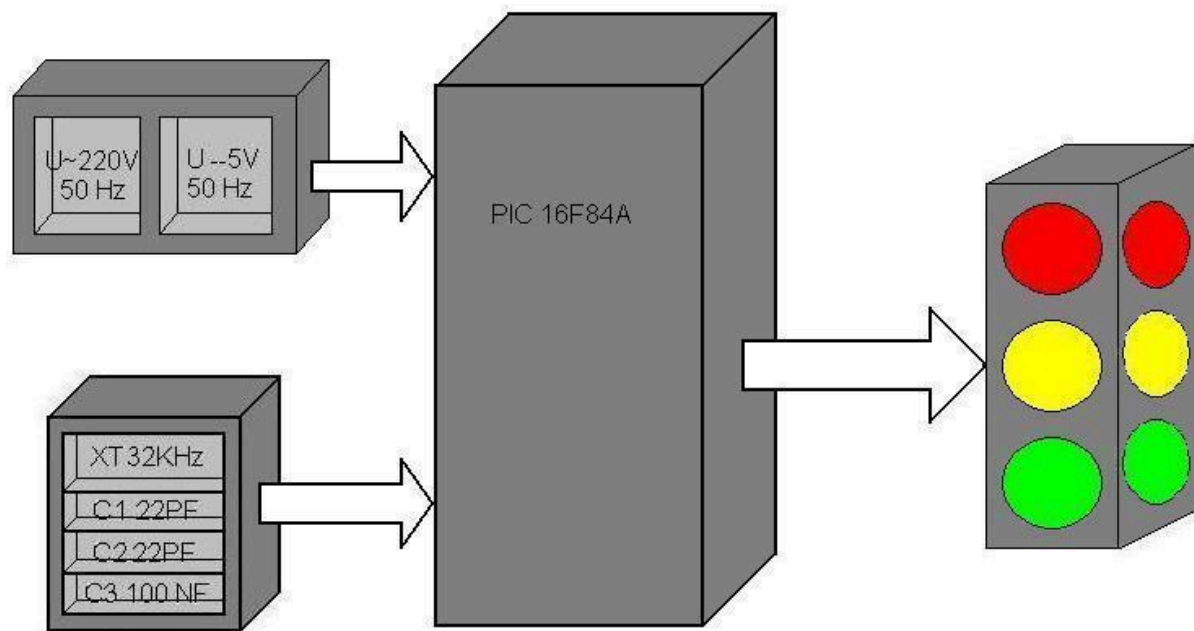

Parts lists

Number	Component	Designation	Symbol	Quantity
0	1	Microcontroller	PIC16F84A	1
1	2	Traffic light system with two sectors	—	1
2	3	Quartz Resonator	X1	1
3	4	Resistor R1	R1	1
4	5	Resistors R2-R7	R2-R7	6
5	6	Capacitor C1	C1	1
6	7	Capacitors C2-C3	C2-C3	2
7	8	LED VD1 & VD4	VD1 & VD4	2
8	9	LED VD2 & VD5	VD2 & VD5	2
9	10	LED VD3 & VD6	VD3 & VD6	2
10	11	Switch	S1	1

Power and Frequency System Schematic

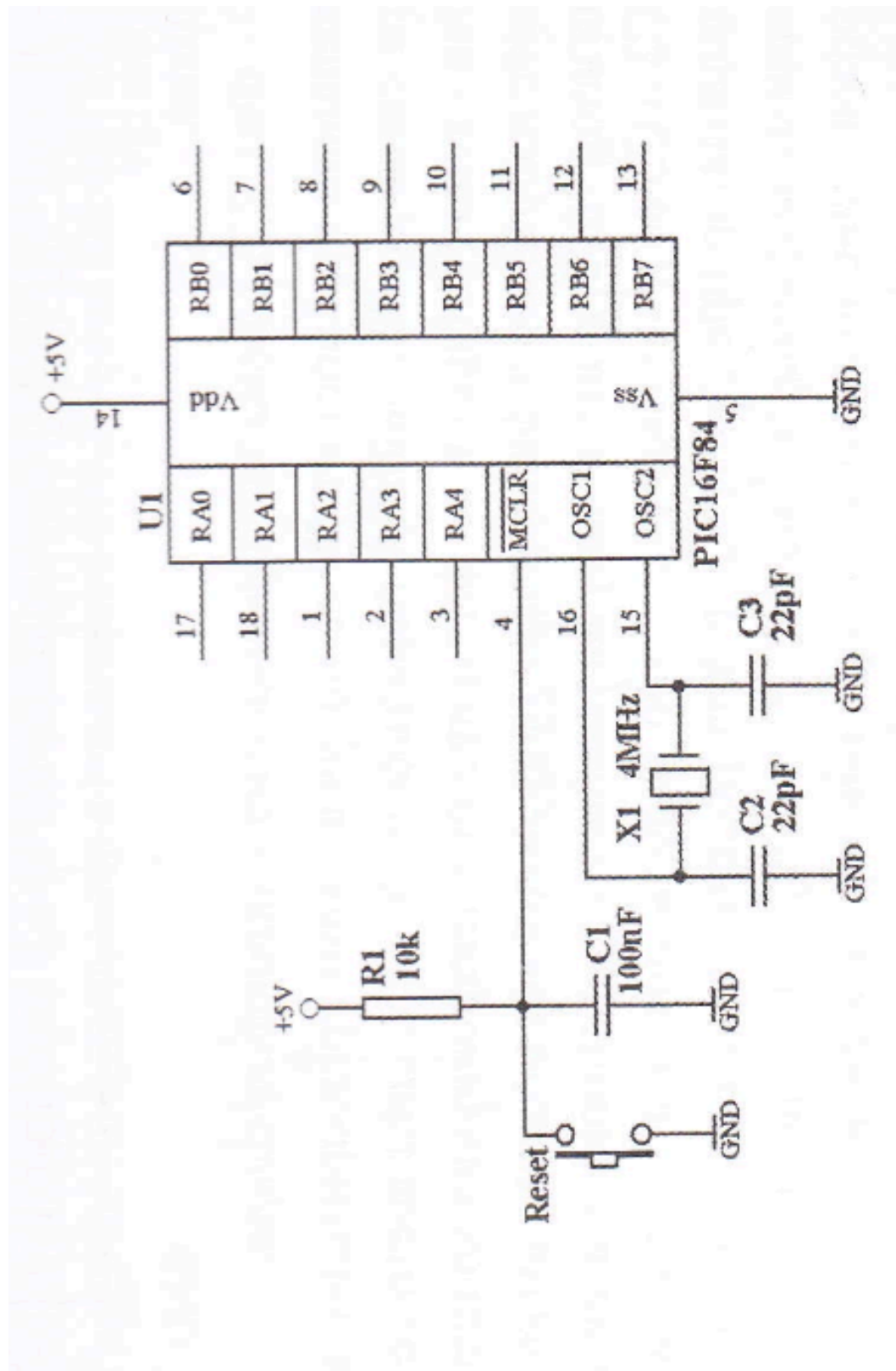

Basic Schematic for Connecting the LEDs

